


# ***The New England Radio Discussion Society's "Electronics for Amateur Radio operators" course***




“Getting down to nuts and volts”

**Phase Two, PPT5  
November 2016**

# Quick review: *L* and *C* in parallel

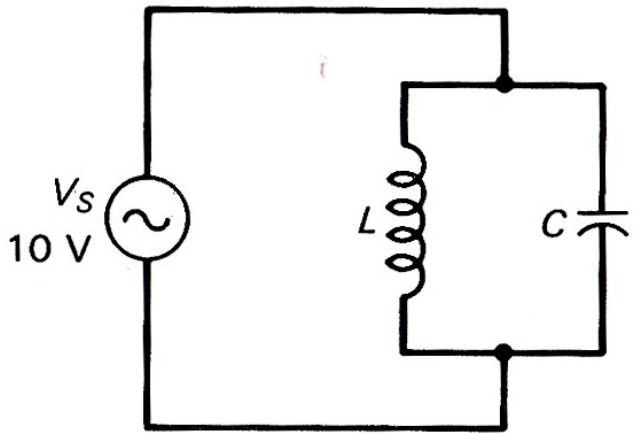


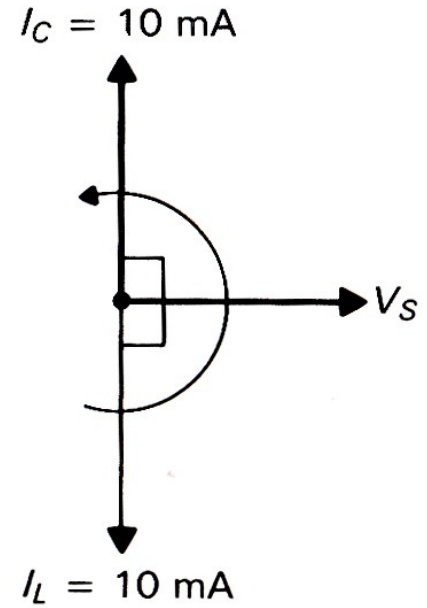
$$X_L = 1 \text{ k}\Omega$$
$$X_C = 1 \text{ k}\Omega$$



**REVIEW: DC  
resistance is in the  
coil windings.**

**That R causes power  
to be dissipated.**

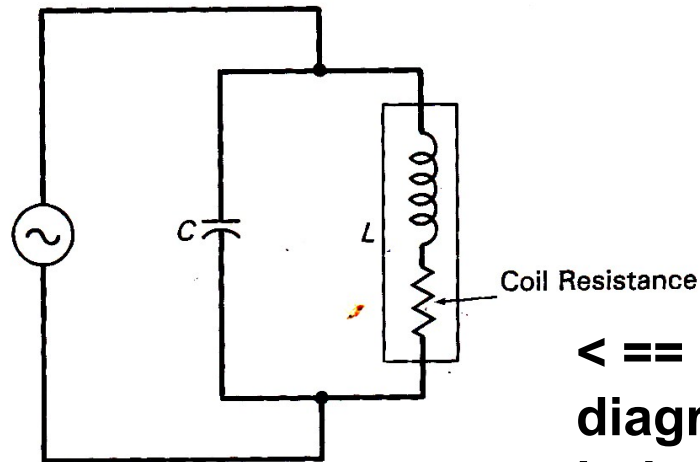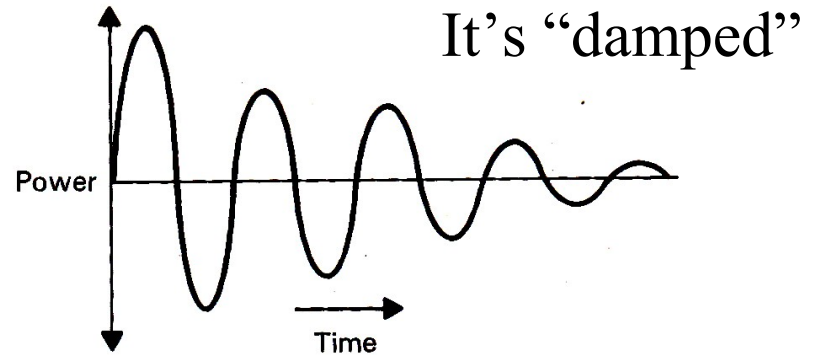**For its part, the  
capacitor has *almost*  
no loss.**




**< == Equivalent  
diagram for the  
inductor**

**REVIEW:** *Impedance (Z)* is the **vector sum** of R and *reactance (X)*, derived from the Pythagorean theorem.

$$C = \sqrt{A^2 + B^2}$$

**Impedance,  $Z = \sqrt{R^2 + X^2}$**

# REVIEW: The vector diagram

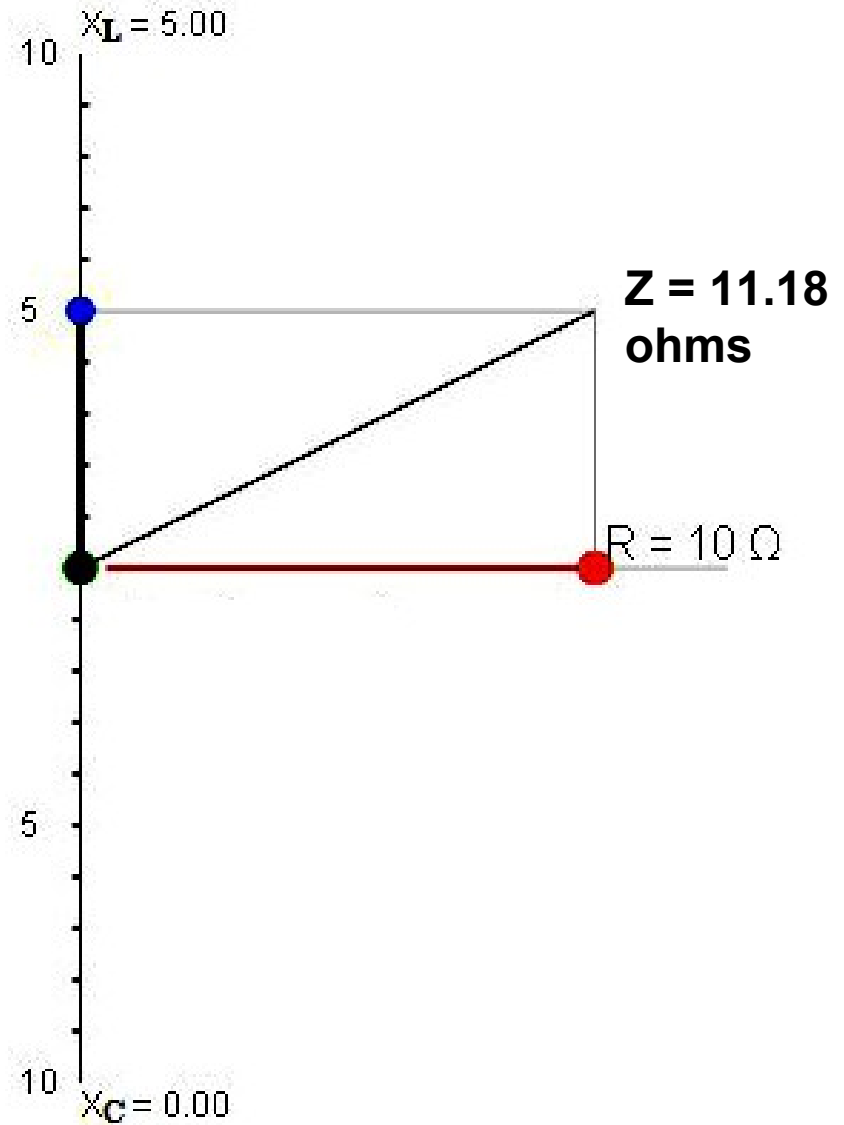

**REVIEW:** The cosine of theta is *power factor*, which indicates dissipated power.

The COS of zero is 1.

The COS of 90 is zero!

In our AC circuits, the power factor is the ratio of the real power that's used to do work, and the *apparent power* that's supplied to a circuit.

When all the power is reactive power with no real power the power factor is 0.


When all the power is real power with no reactive power the power factor is 1.

## REVIEW:

$X_L$  is 10 ohms, and the coil's internal resistance is 2 ohms.

The resultant,  $Z$ , is 10.2 ohms of impedance.

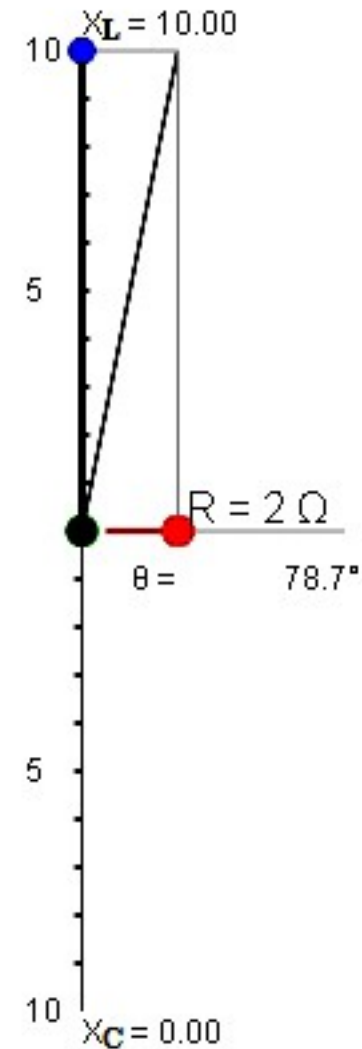The angle is almost 79 degrees. The cosine of theta approaches zero, indicating that there's little power, or heat or light energy, dissipated in this highly inductive circuit.




$Z =$   
10.2  
ohms

**REVIEW: This is an LC circuit.**

**$X_C$  is equal and opposite to its inductive reactance  $X_L$ . Both are 10 ohms.**

**The 10-ohm reactances cancel, as they're equal and opposite, the current and voltage is in phase, and the resultant,  $Z$ , is comprised of resistance only.**

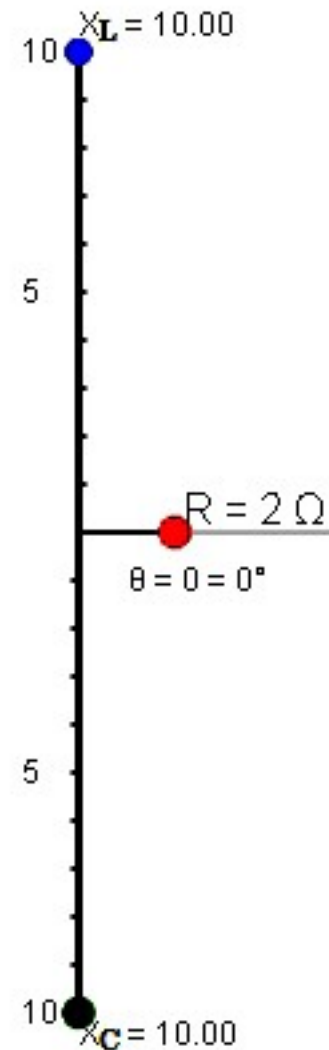**The power factor is the cosine of theta, or 1. The circuit dissipates power in the resistive portion only.**






## REVIEW:

Here  $X_C$  is greater than  $X_L$ .  $X_C$  is 10 ohms and  $X_L$  is 3 ohms.

The capacitive circuit exhibits 12.21 ohms of impedance, and the impedance ( $Z$ ) is capacitive.

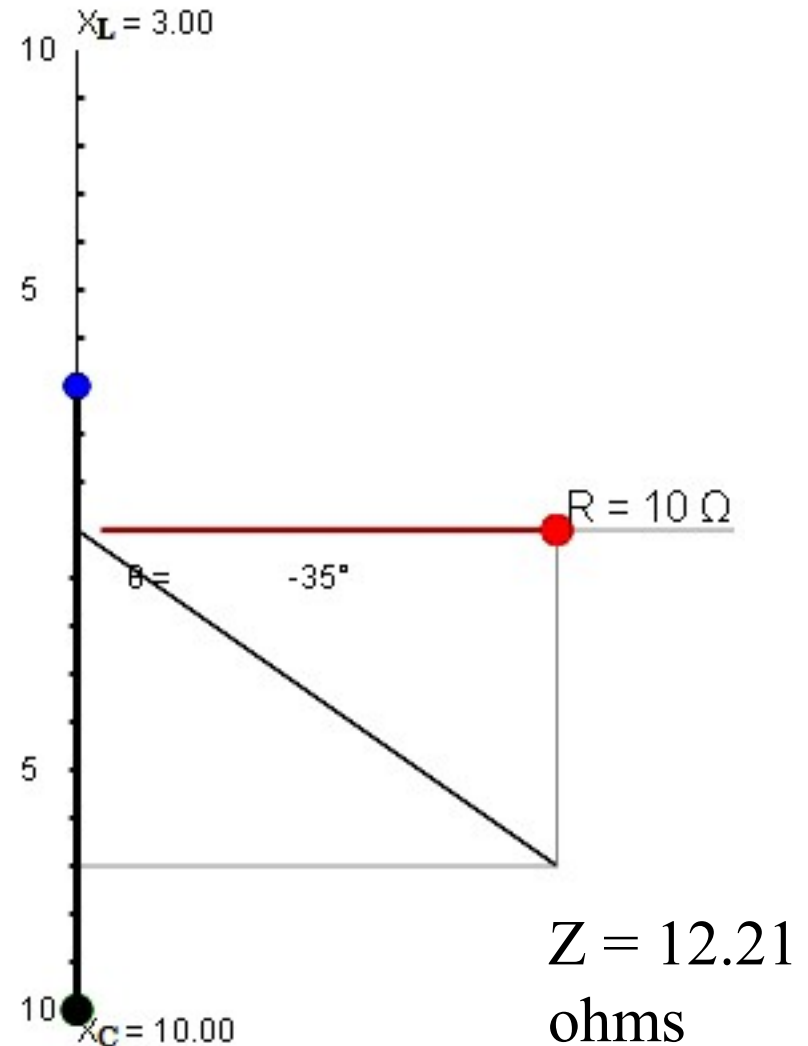The power factor, PF, is 0.81, which is substantial, due to  $R$ .




# Transformers?



**No!**

# Transformers?

## Yes!

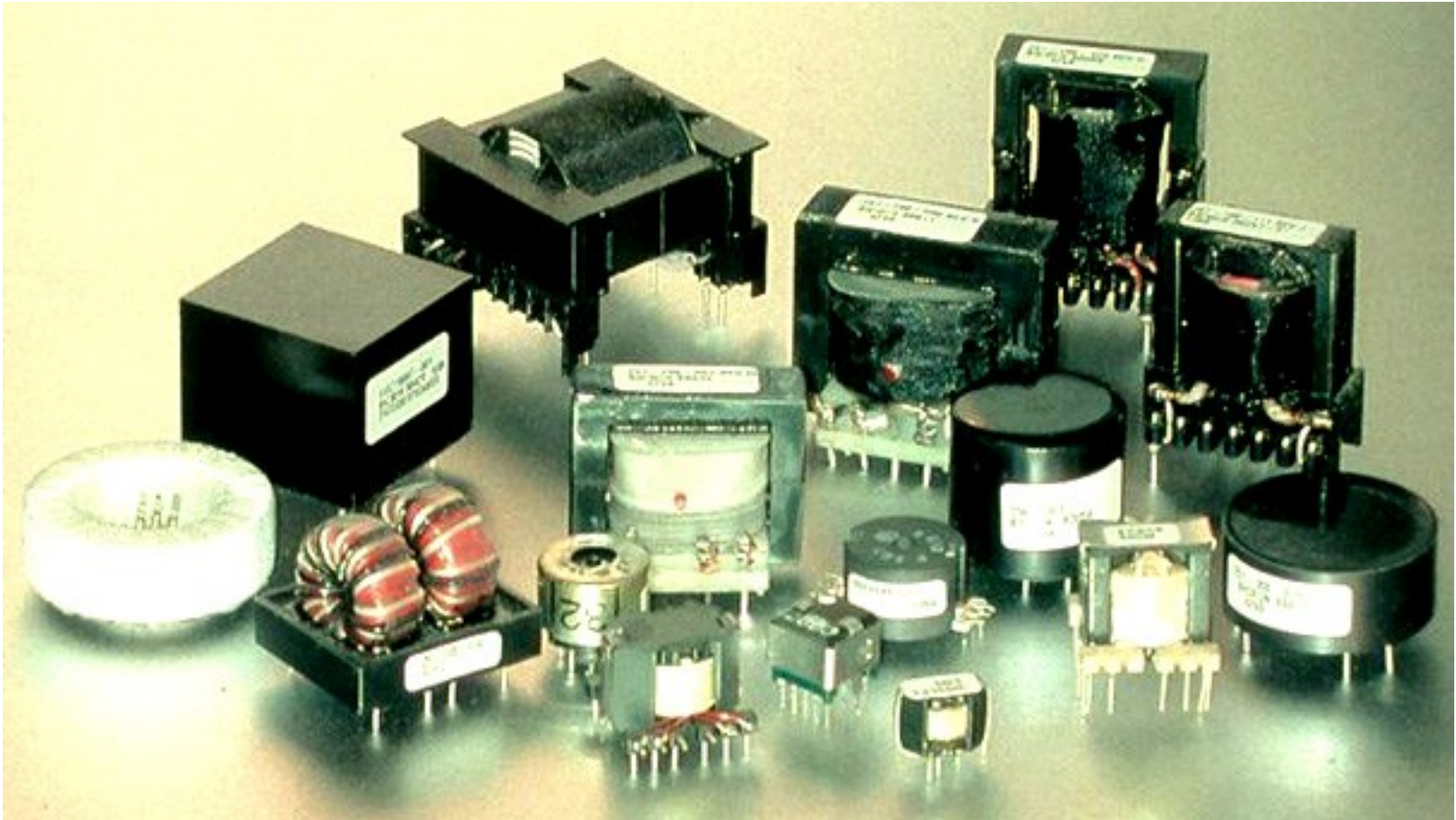

**Primary winding**

$N_p$  turns

Primary current

$I_p$

+

Primary voltage

$V_p$

-

**Secondary winding**

$N_s$  turns

Secondary current


$I_s$

+


Secondary voltage

$V_s$

-

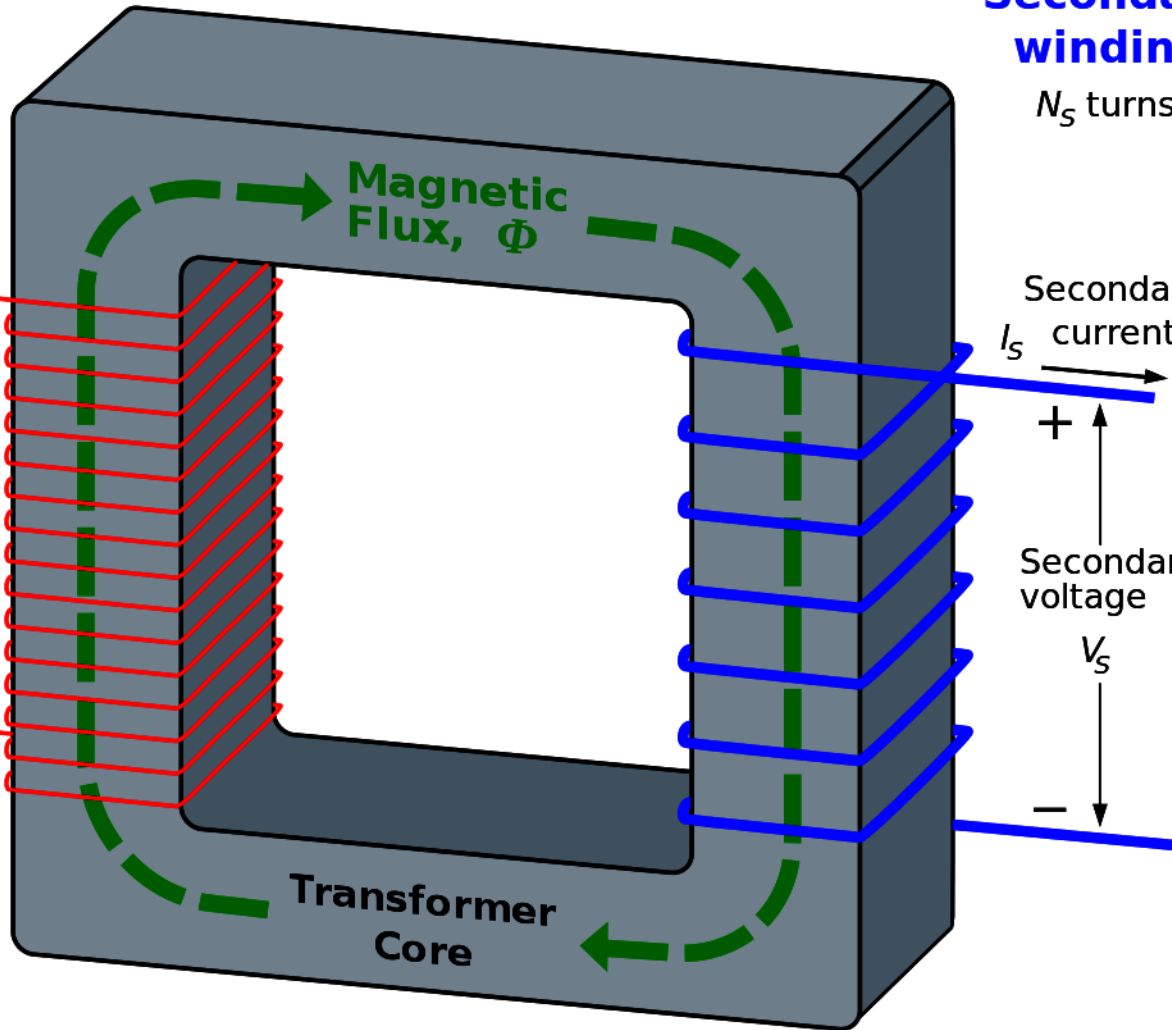


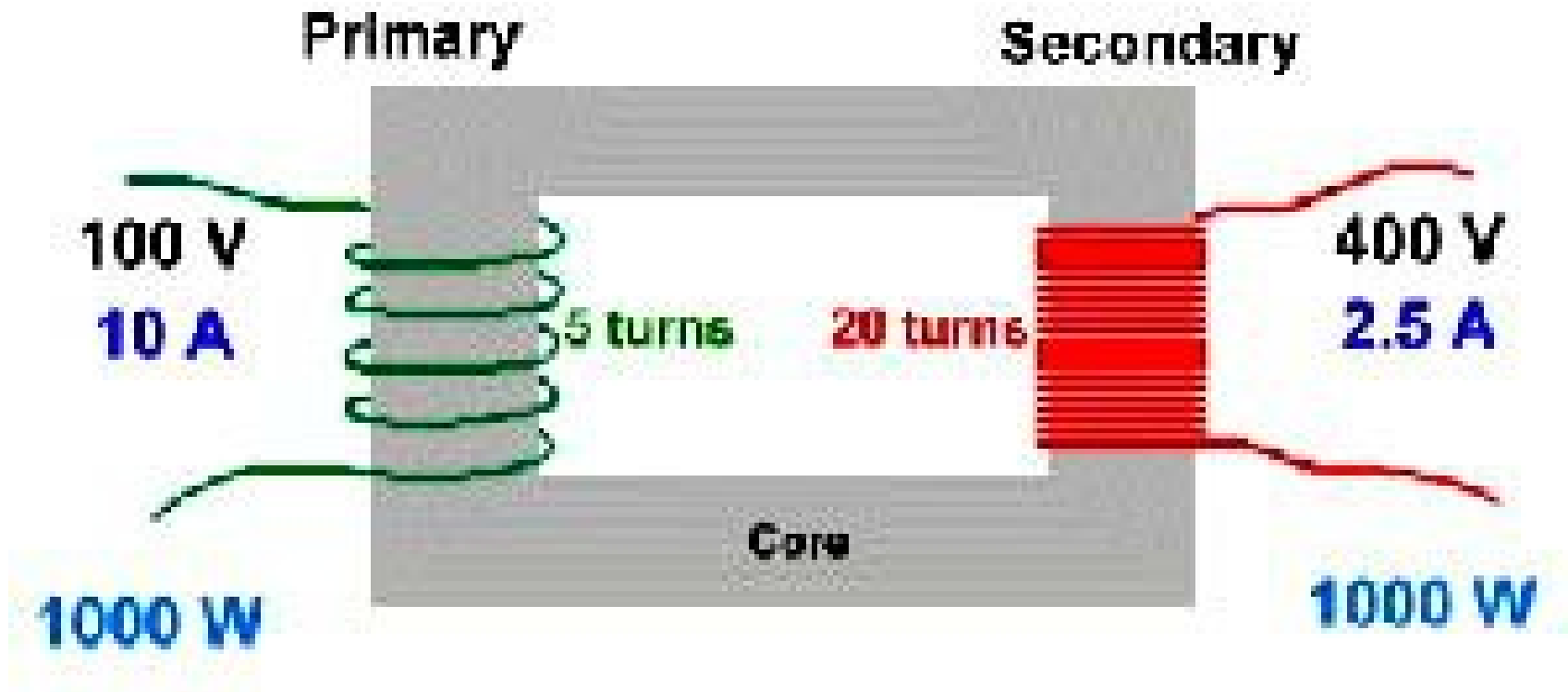This is a “step-up” transformer (XFMR). If the primary and secondary windings were used in reverse, it could be considered a “step-down” transformer.




Transformers are used in AC circuits to step-up and to step-down voltages.

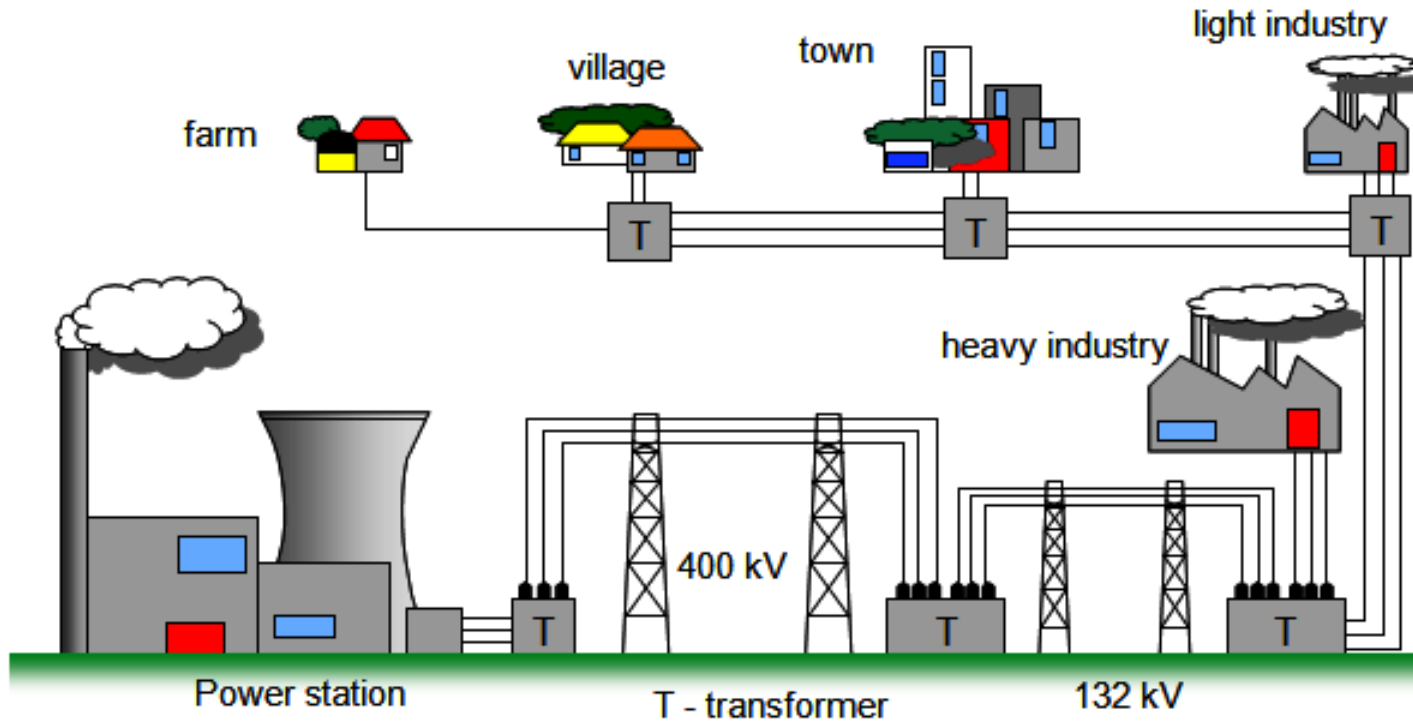In this example the power station delivers 400,000 volts for long distance transmission, which is later stepped down to 132 kV and to 220V.



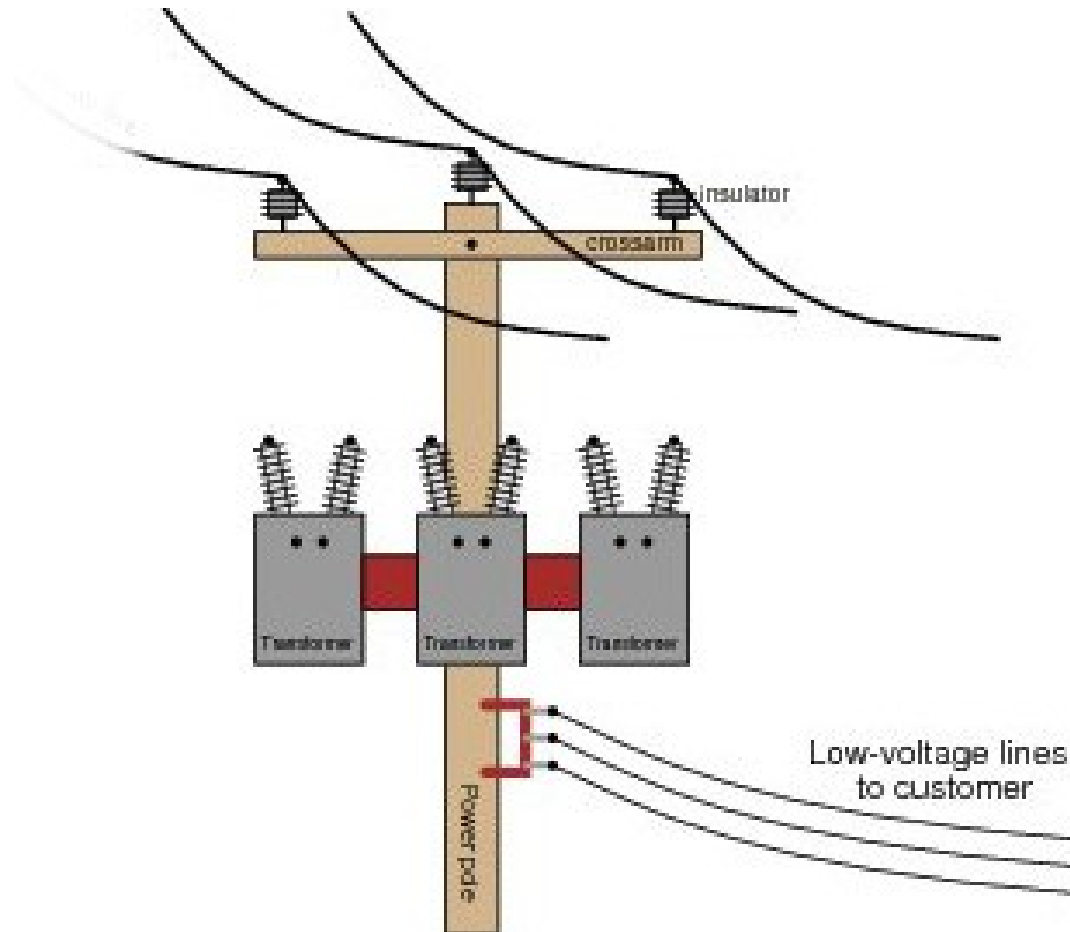**Step-down transformers are used on power poles near your QTH.**






They're sometimes called *pole pigs*.

Hams have actually used these as power transformers in big RF amplifier power supplies.

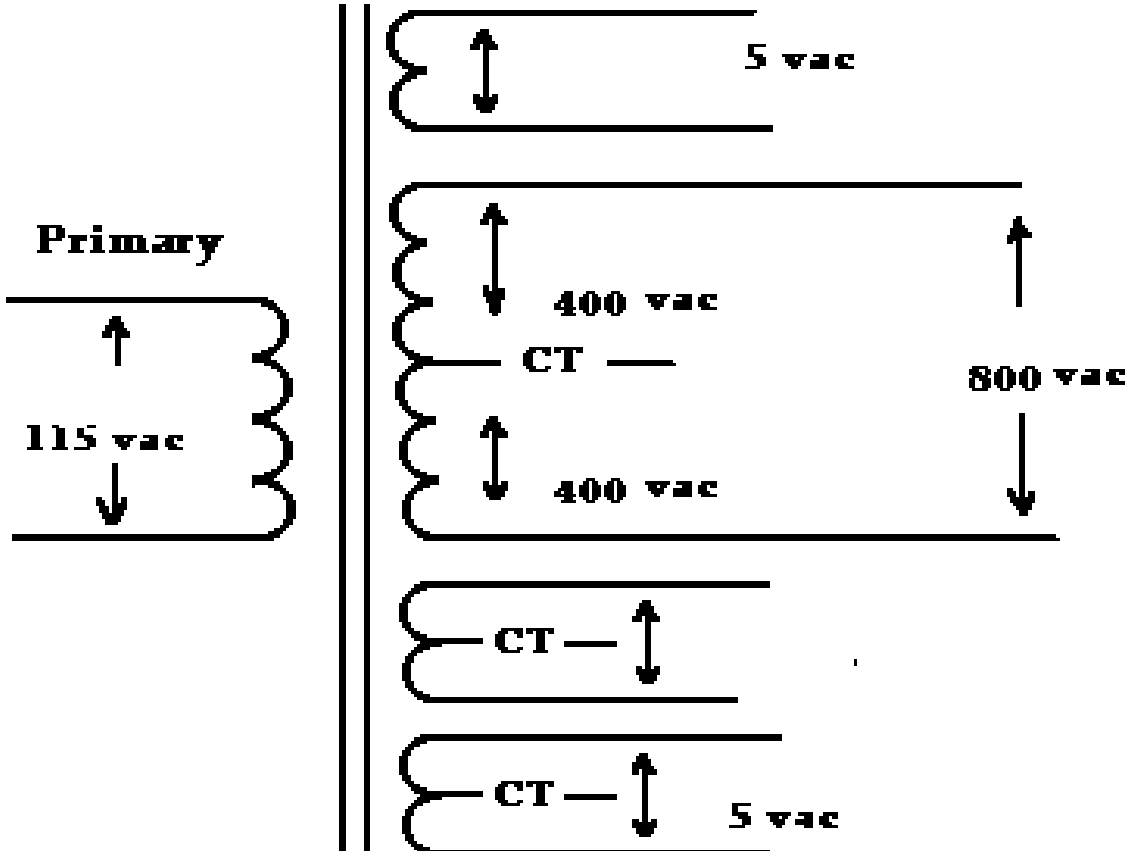**< == *Danger!***




This typical xfmr schematic, used in a ham radio transmitter, has four secondary windings. Three are center-tapped.






**Transformers can also be used to match impedance.**

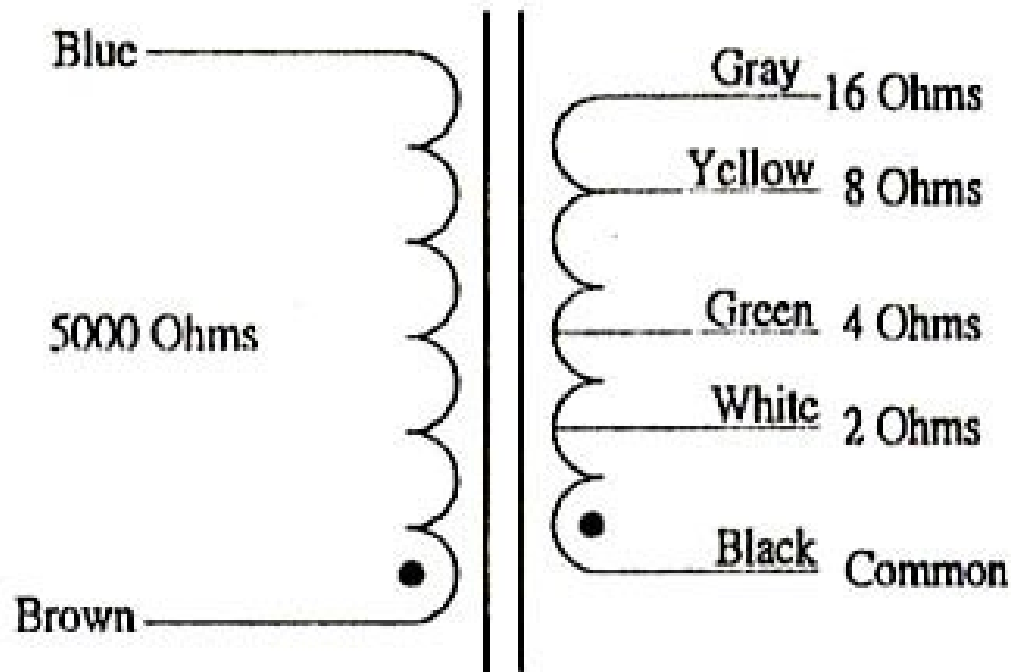**This transformer schematic matches an audio amplifier to a variety of loudspeaker impedances.**



**Transformers work on the principle of mutual induction.**

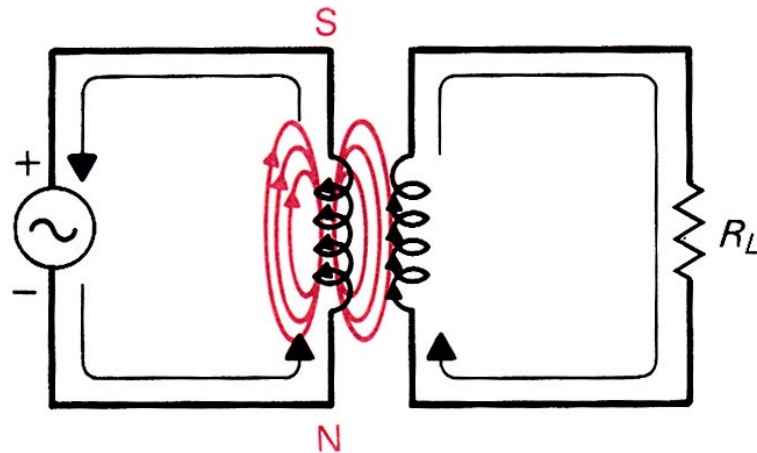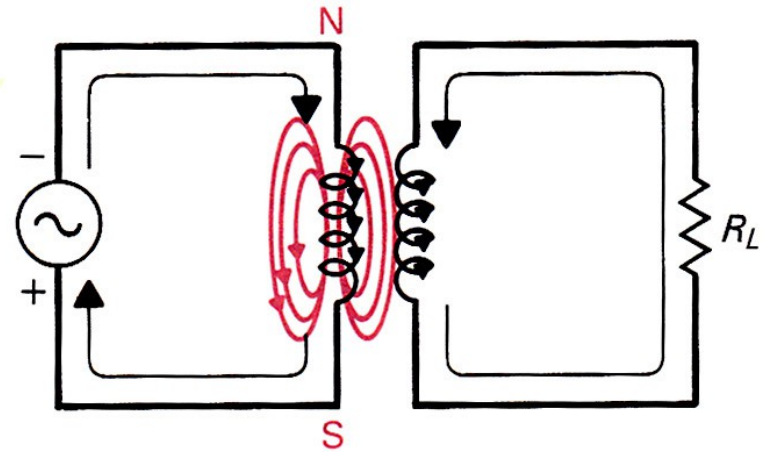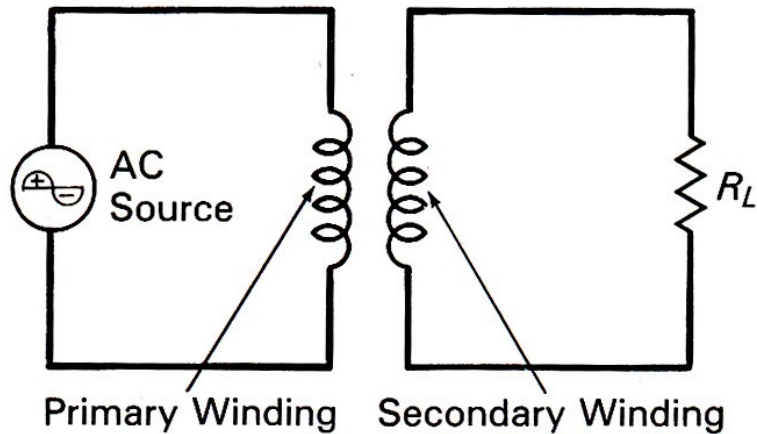**Simply put, if the current in a primary changes, the magnetic flux in the core changes, and the flux that's linked to the secondary changes.**



The AC current in the primary sets up an AC current in the secondary load. The **turns ratio** is the ratio between the number of turns in the primary and the number in the secondary.

The ratio of the secondary voltage to the primary voltage is equal to the *turns ratio*.

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

*Then multiply both sides by  $V_p$  .....*

The re-arranged equation lets you determine the secondary voltage if you know the primary voltage and the turns ratio.

$$V_s = \frac{N_s}{N_p} \times V_p$$


The turns ratio also relates to impedance.

***Impedance matching*** is a prime function of many transformers.


$$\text{turns ratio} = \sqrt{\frac{Z_L}{Z_S}}$$

so,  $(N_p/N_s)^2 = Z \text{ ratio}$

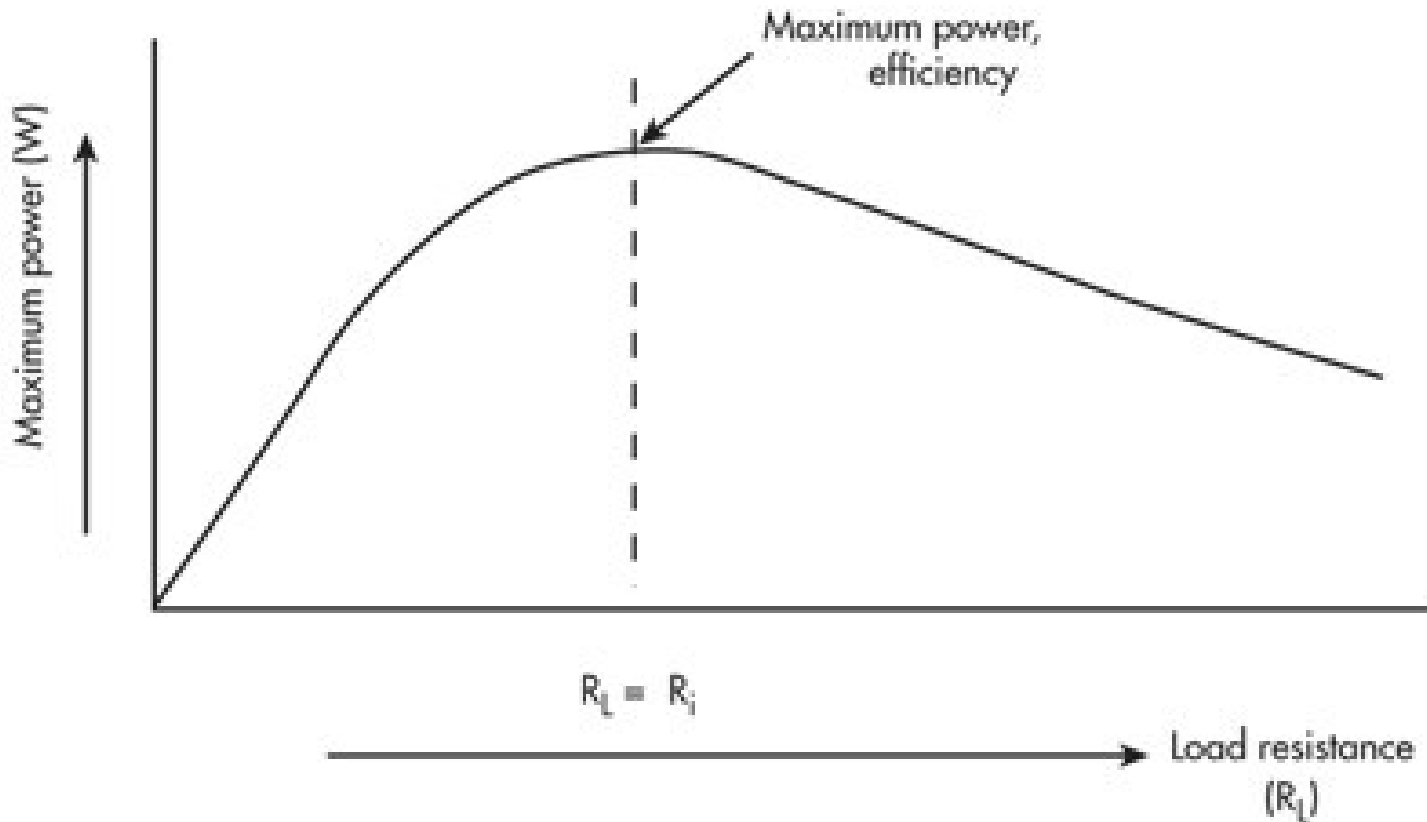
**We know impedance matching is used to match amplifiers to loudspeakers, microphones to rigs, rigs to antennas, etc.**





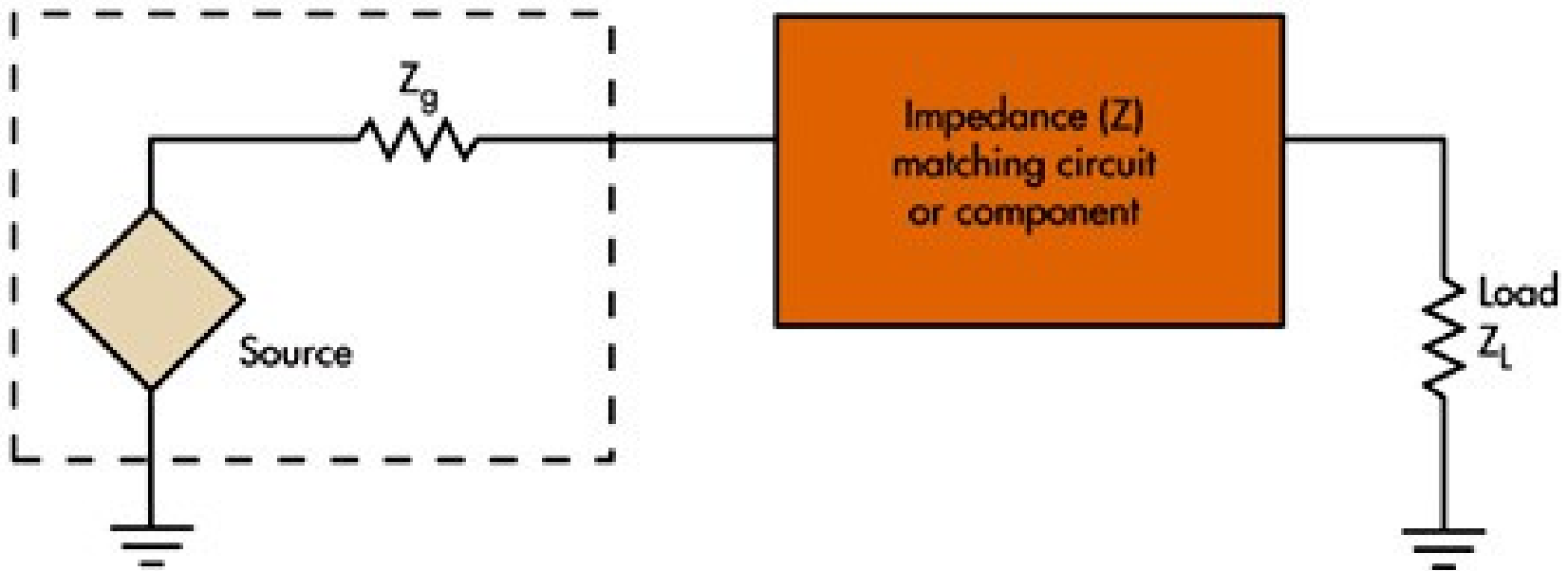

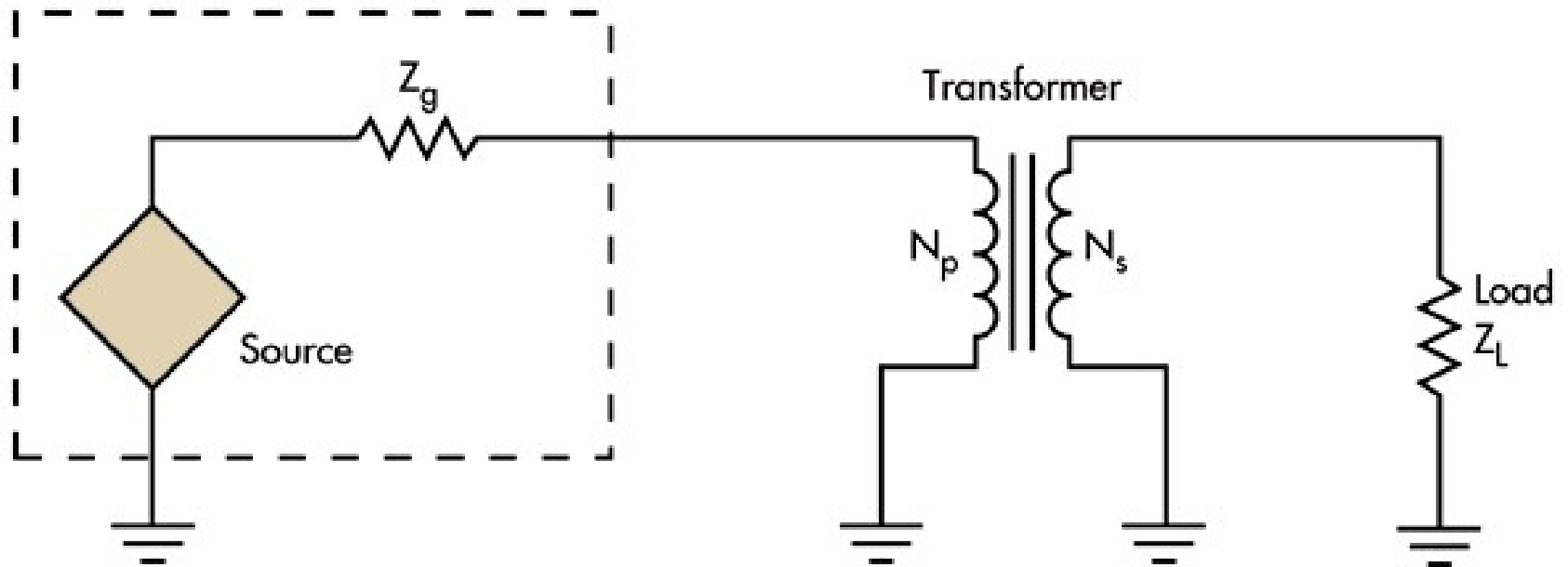**Maximum power transfer occurs when the load is matched to the source.**




$$Z_s/Z_p = (N_s/N_p)^2$$

or:


$$N_s/N_p = \sqrt{Z_s/Z_p}$$

# Enter the auto-transformer!

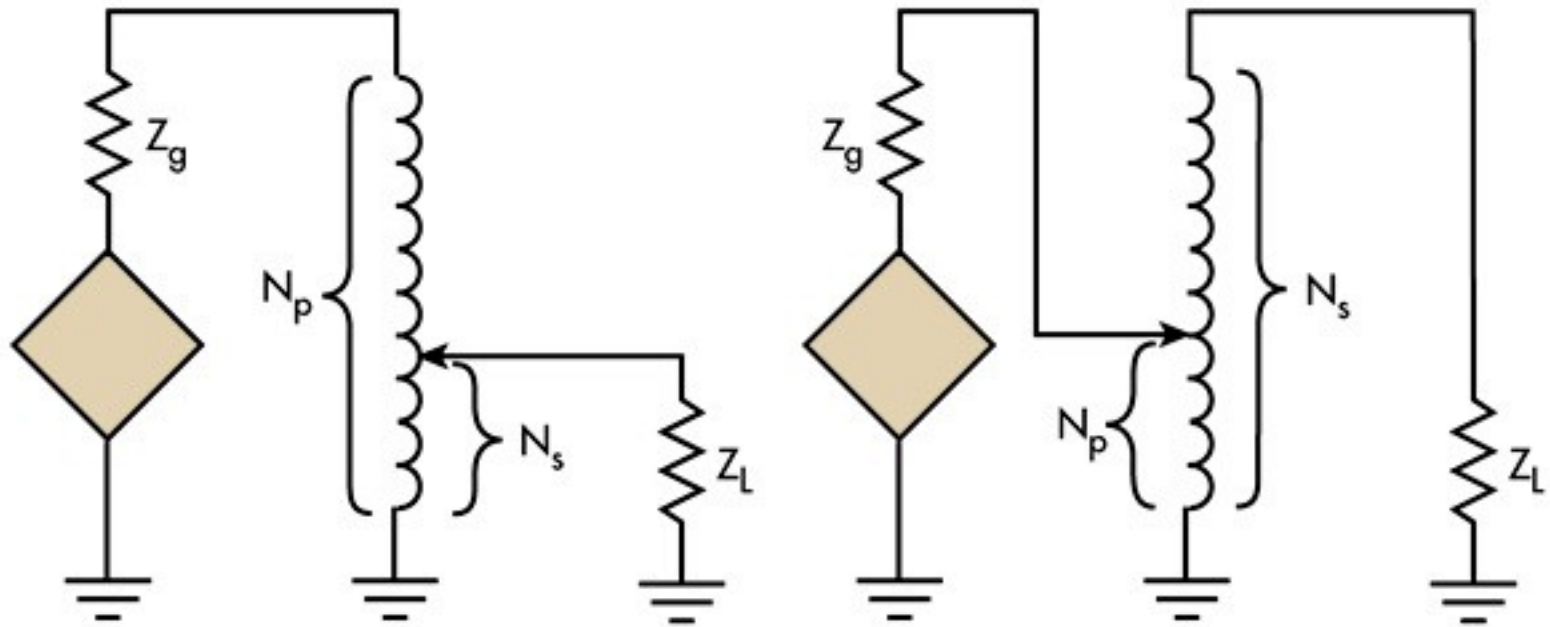

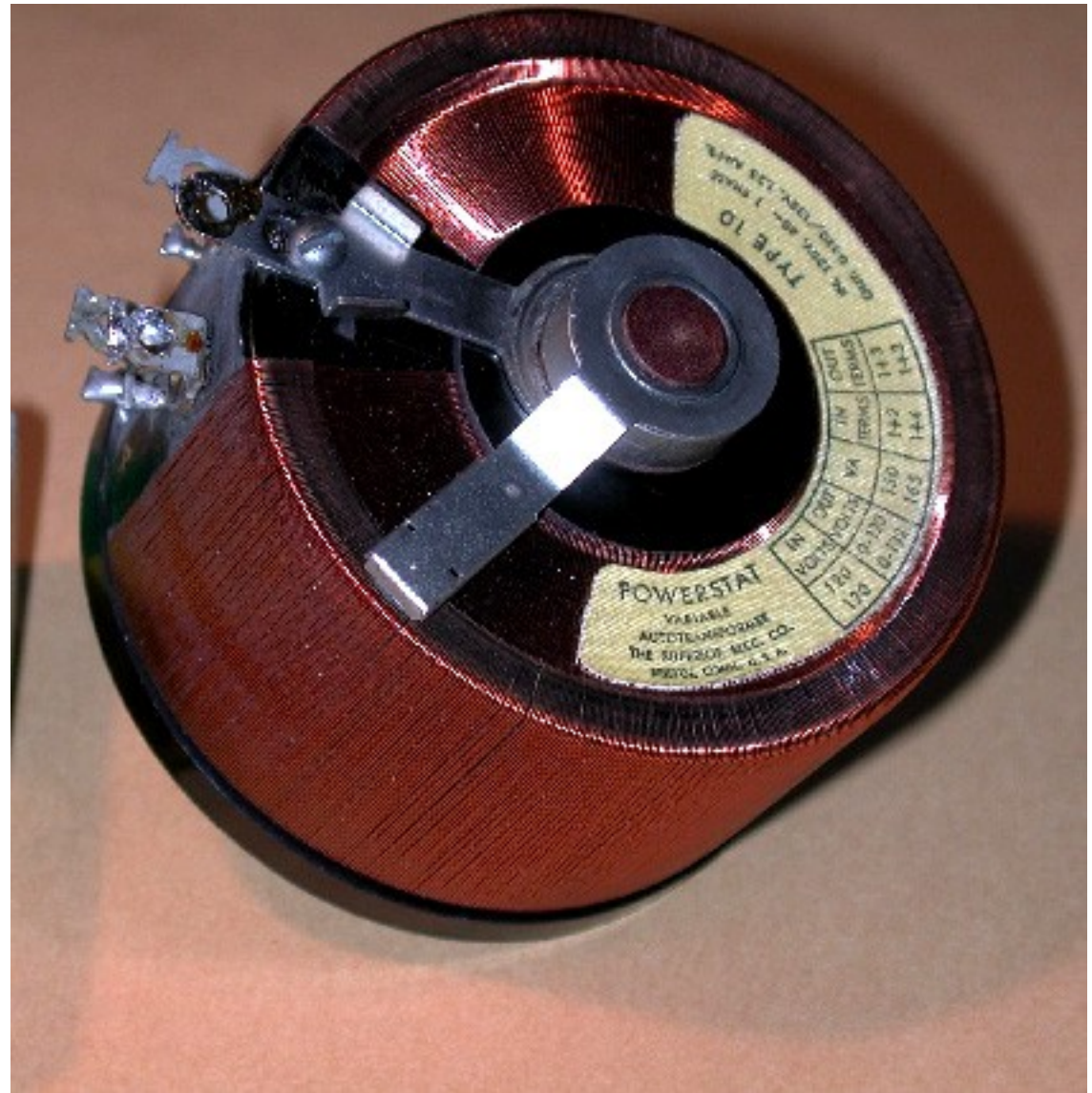
**Auto-transformers are also be used to step-up or step-down voltages.**

**Trade names  
for auto-  
transformers  
have become  
generic, i.e.  
variacs,  
powerstats, etc.**







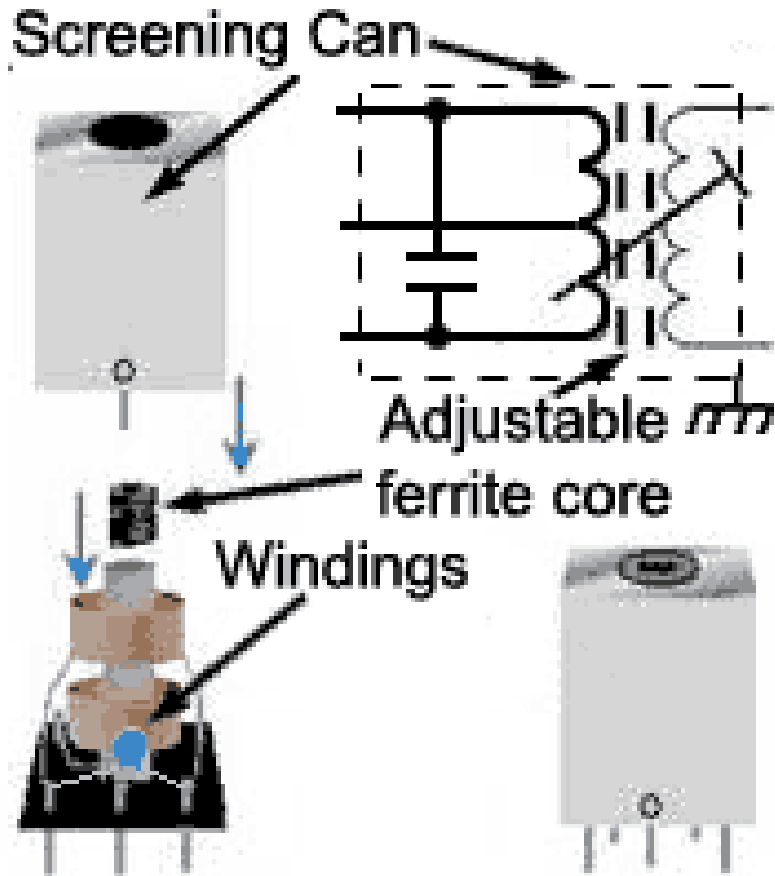Much smaller transformers can be used to couple and match signals in *small-signal* RF circuits.



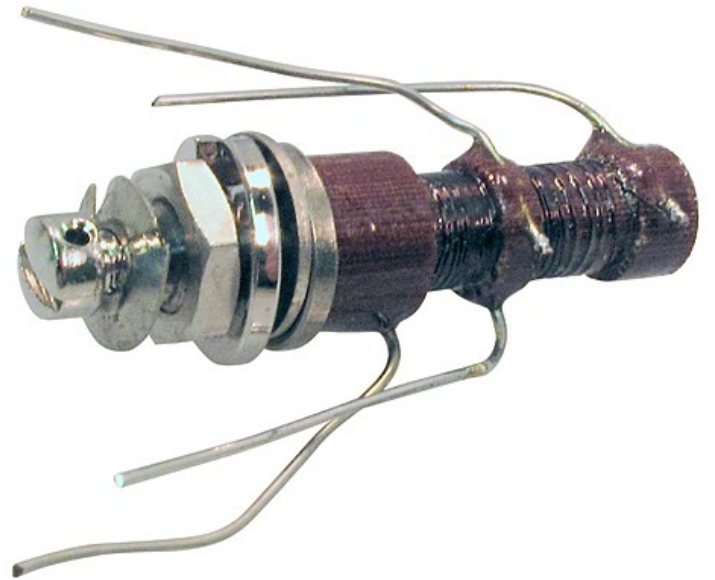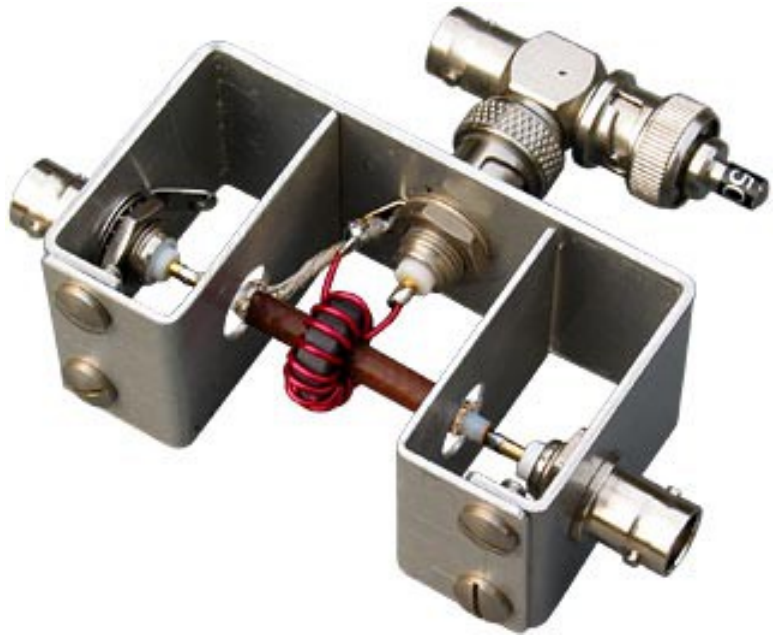This is an example of an intermediate frequency (IF) xfmr, and it's tuned and adjustable.



**If the secondary voltage is stepped up, the secondary current goes down.**

**If the secondary voltage is stepped down, the secondary current goes up.**

**You can't transform more power than you put in!**

**There are also small losses in transformers due to the resistance of the windings, magnetic (hysteresis) losses in the core material, eddy currents, and magnetic leakage.**

**Transformers are VERY efficient – but they're not perfect.**



# *In conclusion ...*



**More to come ...**

73,  
AI2Q, Alex